



PES University, Bangalore
(Established under Karnataka Act No. 16 of 2013)

UE17EC201

SRN

--	--	--	--	--	--	--	--	--	--


DEC 2018: END-SEMESTER ASSESSMENT — B.TECH. IIIrd SEM.
UE17EC201 — NETWORK ANALYSIS & SYNTHESIS

Time: 3 Hrs


Answer All Questions

Max. Marks: 100

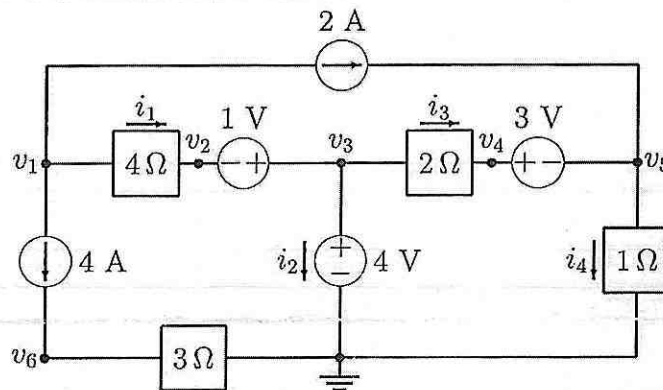
1. (a) Find each of the voltages v_1 through v_6 , the currents i_1 through i_4 , and the power supplied by the 2 A source in the circuit shown below. (7 Marks)



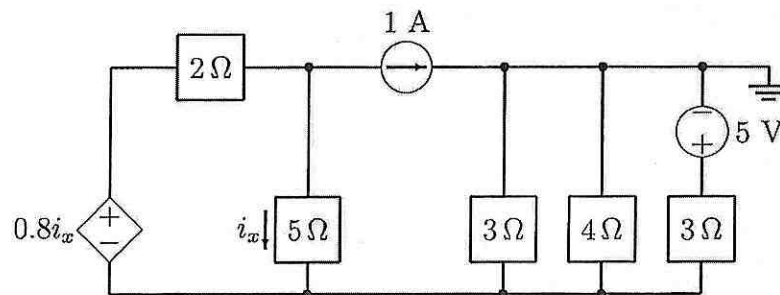- (b) Use mesh analysis to determine the current through each branch of the following circuit. (6 Marks)




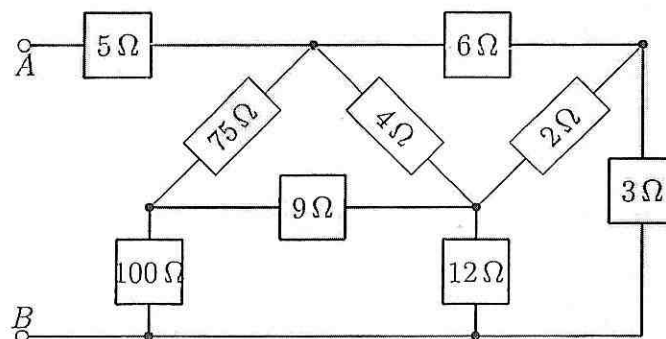- (c) Find the resistance between the terminals A and B. (7 Marks)




2. (a) Find the voltage v_o using the principle of superposition.

(8 Marks)

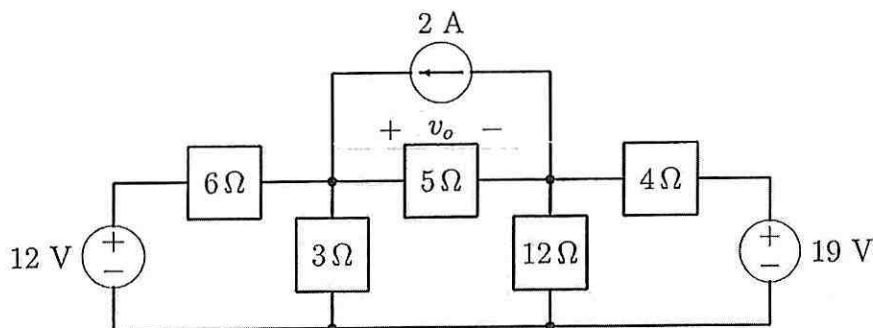


- (b) Find the Thévenin equivalent between the terminals A and B of the circuit shown below:

(4 Marks)

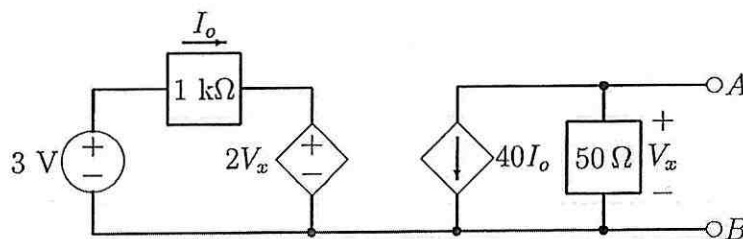

- (c) Find the Norton equivalent between the terminals A and B of the circuit shown below:

(8 Marks)

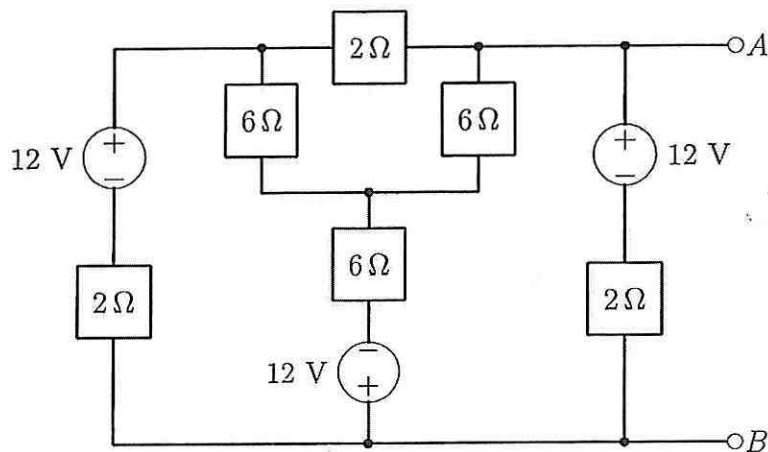

3. (a) A switch is closed at time $t = 0$ connecting a battery of voltage V with a series RC circuit.
- Determine the ratio of energy delivered to the capacitor to the total energy supplied by the source as a function of time.
 - What is the limit of this ratio as $t \rightarrow \infty$.

(8 Marks)