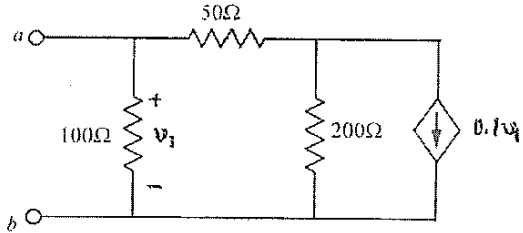
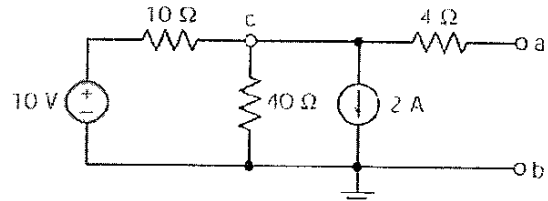
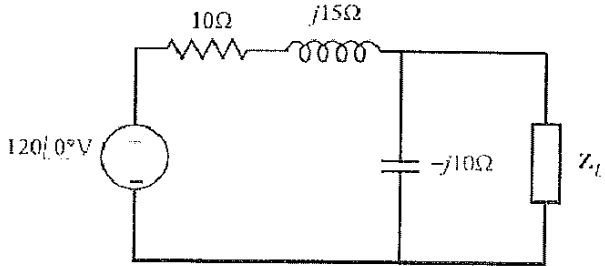
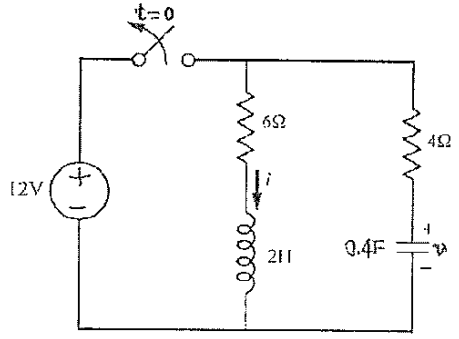


P13

	<p>b. Find Norton's equivalent across terminals ab in the network shown in figure 2b.</p>  <p style="text-align: center;"><b>Figure 2b</b></p>	05
	<p>c. Find Thevinin's equivalent circuit for the network shown in figure 2c across the open circuited terminal.</p>  <p style="text-align: center;"><b>Figure 2c</b></p>	04
	<p>d. What is the value of load impedance <math>Z_L</math> that will absorb the maximum average power? What is the value maximum power absorbed?</p>  <p style="text-align: center;"><b>Figure 2d</b></p>	06
3	<p>a. A series RL circuit is connected in series with a battery of 12V and switch 'k'. Switch k is closed at <math>t = 0</math>. Assuming zero initial current in the inductor, find the values <math>i(0+)</math>, <math>\frac{di}{dt}(0+)</math> and <math>\frac{d^2i}{dt^2}(0+)</math>. Value of <math>R = 8\Omega</math> and <math>L = 0.2H</math>.</p> <p>b. Referring to the circuit shown in figure 3b, the switch was closed for long time before it was open at <math>t = 0</math>. Find the following,</p> <ol style="list-style-type: none"> <li><math>i(0+)</math> and <math>v(0+)</math></li> <li><math>\frac{di}{dt}(0+)</math> and <math>\frac{dv}{dt}(0+)</math></li> <li><math>i(\infty)</math> and <math>v(\infty)</math></li> </ol>  <p style="text-align: center;"><b>Figure 3b</b></p>	05 09
	<p>c. Find time domain solution for <math>V_o</math> applicable for <math>t \geq 0</math> in the circuit of figure 3c</p>	06

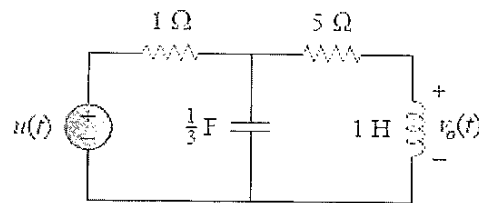


Figure 3c

- 4 a. Find  $Y_{12}$  and  $Y_{21}$  for the circuit shown below for  $n = 10$ . What is the value of  $n$  for circuit to be reciprocal?

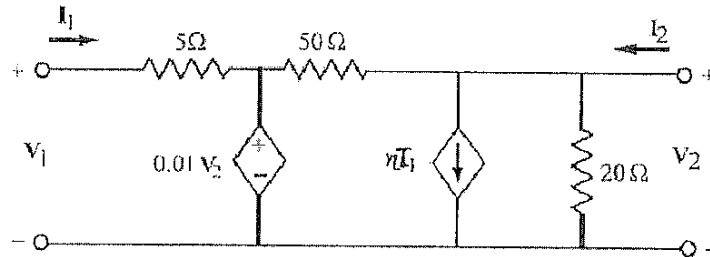


Figure 4a

- b. Using the concept of interconnection of two port networks, find T-parameters of the network shown in figure 4b.

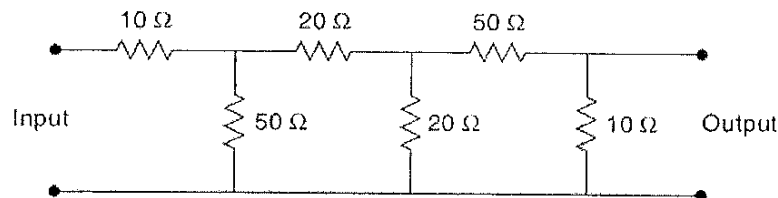


Figure 4b

- c. The h-parameters of the two-port network are given. Find the y – parameters for the network.

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 5 & 2 \\ 3 & 6 \end{bmatrix}$$

- 5 a. Find whether the following functions are realizable and give reason for your answer.

i)  $Z(s) = s^2 + 1$

ii)  $Z(s) = \frac{s^2 + 1}{s^3}$

- b. Synthesize the Foster I form and Foster II form for the network function

$$Z(s) = \frac{s(s^2 + 2)}{(s^2 + 1)(s^2 + 3)}$$

- c. List out the properties of LC immittance function and then realize the network having the driving point impedance function  $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$  using cauer I form.