



**DECEMBER 2020: END SEMESTER ASSESSMENT (ESA), B.TECH**  
**CMOS Analog Circuit Design**

Time: 3 Hrs



Answer All Questions



Max Marks: 100

SRN 

--	--	--	--	--	--	--	--	--	--

1	a)	Derive an expression for the drain current of a n-channel MOSFET.	7
	b)	Calculate the bias current of $M_1$ in Fig. 1.b. Assume $\mu_n C_{ox} = 100 \mu A/V^2$ and $V_{th} = 0.4 V$ . If the gate voltage increases by 10 mV, what is the change in the drain voltage?	6
	c)	Based on the value of $V_{DS}$ , write the large signal models of a n-channel MOSFET	7
2	a)	Derive an expression for the small signal gain of a common source amplifier with resistive load.	7
	b)	In the circuit of Fig. 2.b, determine the maximum allowable value of $W/L$ if $M_1$ must remain in saturation. Assume $\lambda = 0$ . Assume $\mu_n C_{ox} = 200 \mu A/V^2$ and $V_{th} = 0.4 V$ .	6
	c)	Explain the large signal behavior of a common gate amplifier, hence obtain the transfer characteristics for the same.	7
3	a)	Explain the differential input-output characteristics of a MOSFET differential pair.	7
	b)	With neat circuit diagram obtain an expression for common mode gain of a differential pair sensing Common Mode input.	6

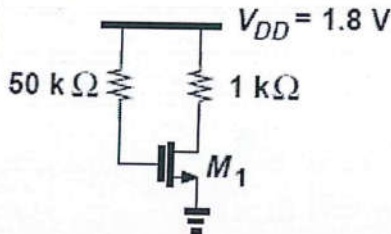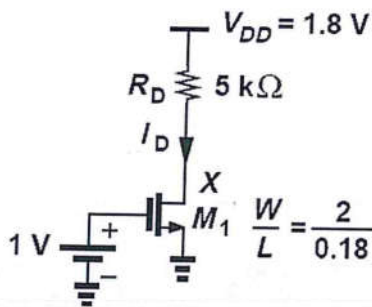

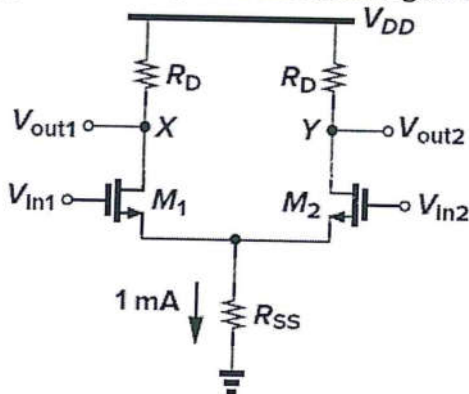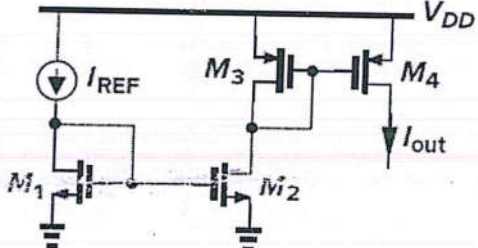c)	<p>The circuit of Fig. 3.c. uses a resistor rather than a current source to define a tail current of 1 mA. Assume that <math>(W/L)_{1,2} = 25/0.5</math>, <math>\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2</math>, <math>V_{TH} = 0.6 \text{ V}</math>, <math>\lambda = \gamma = 0</math>, and <math>V_{DD} = 3 \text{ V}</math>.</p> <p>(a) What is the required input CM voltage for which <math>R_{SS}</math> sustains 0.5 V?</p> <p>(b) Calculate <math>R_D</math> for a differential gain of 5.</p> 	7
4 a)	With neat circuit diagram explain about the voltage headroom consumed by the cascode current mirror circuit.	7
b)	<p>In Fig. 4.b, find the drain current of <math>M_4</math> if all of the transistors are in saturation.</p> 	6
c)	Derive an expression for the short-circuit transconductance, $G_m$ , and the output resistance, $R_{out}$ for the differential pair with current-source load.	7
5 a)	Get an expression for the transfer function of high-frequency model of a common-source stage, using Miller's approximation.	7
b)	Explain how to determine the loop gain in a simple feedback circuit.	6
c)	Show that the input impedance will be modified with feedback for a Common-gate circuit.	7