
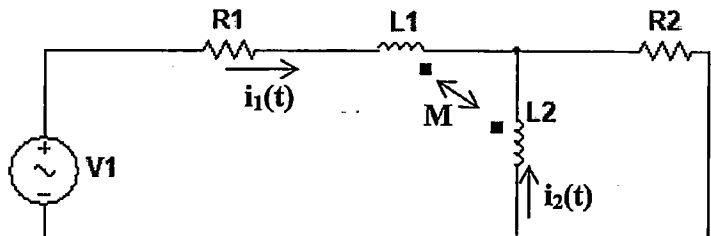
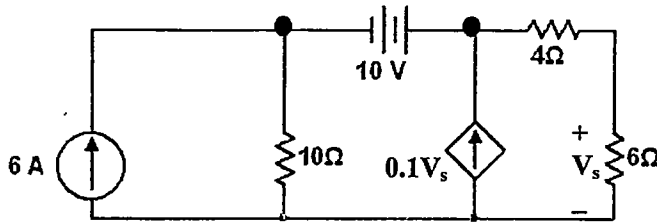
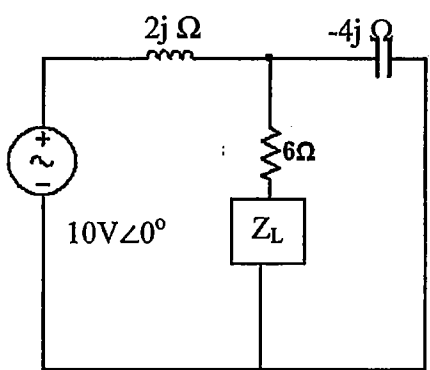



DECEMBER 2016: END SEMESTER ASSESSMENT (ESA) B.TECH. III SEMESTER

UE15EC201- Network Analysis and Synthesis

Time: 3 Hrs		Answer All Questions	Max Marks: 100
1.	a)	State four differences between nodal analysis and mesh analysis	4
	b)	Answer the following. <ul style="list-style-type: none"> i. Suppose the transformer is ideal. Suppose it has one primary winding and one secondary winding. How is the mutual inductance M related to the self inductances L_1 and L_2? ii. Suppose L_1 is 2 H and M is 0.6 H, what is the value of L_2? 	4
	c)	Write the mesh equations for the circuit given below 	6
	d)	Find the values of the nodal voltages (at the dark circles) in the given circuit using the concept of super node. Find the power contribution of the dependent source. 	6
2.	a)	Find the Norton's equivalent circuit across the load Z_L . 	4
	b)	For the circuit given below, find the maximum power that can be dissipated by the load resistance R_L which is variable (note the load reactance is zero). Find the optimal value of R_L . Write appropriate formula in the calculation.	6

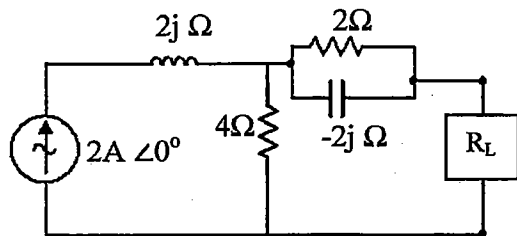


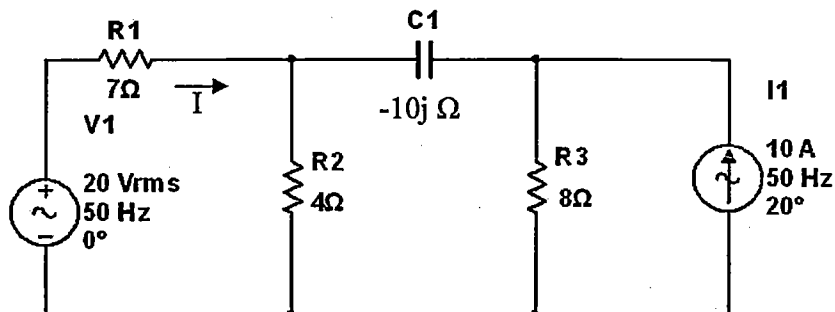- c) Apply superposition theorem to find the current flowing through the resistance R_L



- d) State Millman's Theorem using appropriate expressions.

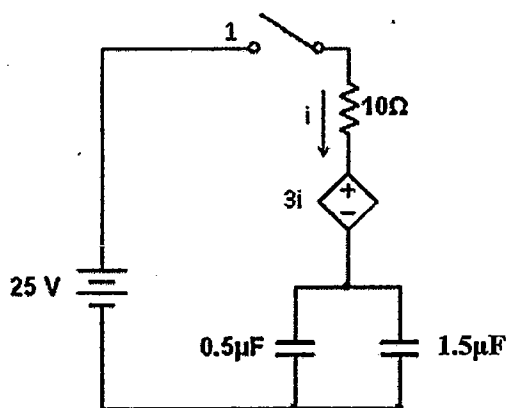3. a) The switch was open for a long time before it moves to position 1 at $t=0$. For the circuit given below find the transient current $i(t)$ for $t > 0$.



- b) Suppose a series RL circuit is excited by a current source of 1A at $t=0$. Suppose if the value of $R=10$ Ohms. Find the value of L such that the transient voltage across the inductor reaches 3V at 3ms. Explain your calculation.

- c) Consider a source free series RLC circuit having $R = 10 \Omega$, $\omega_0 = 1000$ rad/s and damping ratio $\zeta = 1.5$. Suppose the initial values are $v_c(0^+) = 10$ V and $\frac{dv_c(0^+)}{dt} = -3$ V/s.

- Find the values of L and C .
- Find the transient voltage $v_c(t)$ across the capacitor for $t \geq 0$.
- Without changing L and C , what value of R will make the circuit critically damped?

4. a) Determine the y parameters of the two port network using nodal analysis. Based on the y parameters, calculate the parameter z_{11} .

